

Design and Simulation of Single-Stage MOS Differential Amplifier with Active Load

Laboratory Report


M.B.S Aravind
EE24BTECH11038

July 16, 2026

The differential amplifier is one of the most fundamental building blocks in analog integrated circuit design. This experiment focuses on designing and simulating a single-stage CMOS differential amplifier with an active current-mirror load to achieve high differential gain, good common-mode rejection, and superior performance characteristics compared to passive resistive loads.

The primary objectives of this laboratory experiment are:

- ### 3 Cirucit

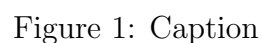

4 DC Operating Point Analysis

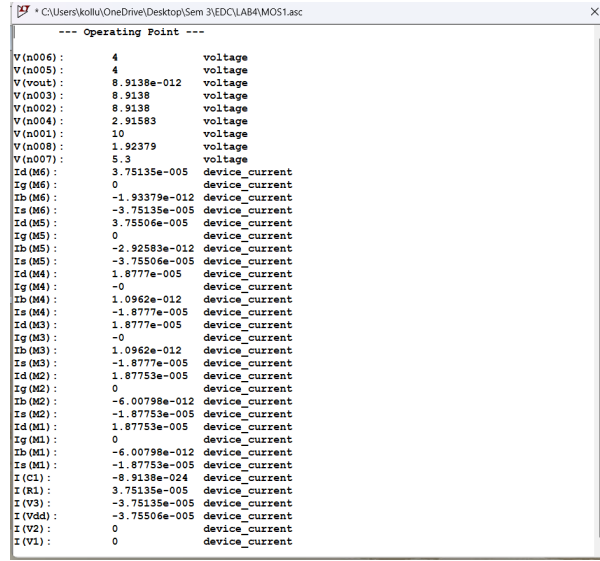


Figure 2: Caption

5 Current Analysis

5.1 Transistor M1 and M2 (NMOS - Differential Pair)

$$V_G = 4 \text{ V} \quad (1)$$

$$V_S = 2.91583 \text{ V} \quad (2)$$

$$V_D = 8.9138 \text{ V} \quad (3)$$

$$V_{TH} = 1.0 \text{ V} \quad (4)$$

$$V_{GS} = V_G - V_S = 4 - 2.91583 = 1.08417 \text{ V} \quad (5)$$

$$V_{DS} = V_D - V_S = 8.9138 - 2.91583 = 5.99797 \text{ V} \quad (6)$$

Saturation Check:

$$V_{GS} > V_{TH} \Rightarrow 1.08417 \text{ V} > 1.0 \text{ V} \quad \checkmark \quad (7)$$

$$V_{DS} > V_{GS} - V_{TH} \Rightarrow 5.99797 \text{ V} > 0.08417 \text{ V} \quad \checkmark \quad (8)$$

M1 and M2 are in SATURATION

5.2 Transistor M3 and M4 (PMOS - Current Mirror Load)

$$V_G = V_D = 8.9138 \text{ V} \quad (9)$$

$$V_S = 10 \text{ V} \quad (10)$$

$$V_{TH} = -1.0 \text{ V} \quad (11)$$

$$V_{SG} = V_S - V_G = 10 - 8.9138 = 1.0862 \text{ V} \quad (12)$$

$$V_{SD} = V_S - V_D = 10 - 8.9138 = 1.0862 \text{ V} \quad (13)$$

Saturation Check:

$$V_{SG} > |V_{TH}| \Rightarrow 1.0862 \text{ V} > 1.0 \text{ V} \quad \checkmark \quad (14)$$

$$V_{SD} > V_{SG} - |V_{TH}| \Rightarrow 1.0862 \text{ V} > 0.0862 \text{ V} \quad \checkmark \quad (15)$$

M3 and M4 are in SATURATION

5.3 Transistor M5 (NMOS - Tail Current Source)

$$V_G = 1.92379 \text{ V} \quad (16)$$

$$V_S = 0 \text{ V} \quad (17)$$

$$V_D = 2.91583 \text{ V} \quad (18)$$

$$V_{TH} = 0.7 \text{ V} \quad (19)$$

$$V_{GS} = 1.92379 \text{ V} \quad (20)$$

$$V_{DS} = 2.91583 \text{ V} \quad (21)$$

Saturation Check:

$$V_{GS} > V_{TH} \Rightarrow 1.92379 \text{ V} > 0.7 \text{ V} \quad \checkmark \quad (22)$$

$$V_{DS} > V_{GS} - V_{TH} \Rightarrow 2.91583 \text{ V} > 1.22379 \text{ V} \quad \checkmark \quad (23)$$

M5 is in SATURATION

5.4 Transistor M6 (NMOS - Current Mirror Reference)

$$V_G = V_D = 1.92379 \text{ V} \quad (\text{diode-connected}) \quad (24)$$

$$V_S = 0 \text{ V} \quad (25)$$

$$V_{TH} = 0.7 \text{ V} \quad (26)$$

$$V_{GS} = 1.92379 \text{ V} \quad (27)$$

Saturation Check:

$$V_{GS} > V_{TH} \Rightarrow 1.92379 \text{ V} > 0.7 \text{ V} \quad \checkmark$$

M6 is in SATURATION

Aspect Ratios:

$$\left(\frac{W}{L}\right)_{M1,M2,M3,M4,M6} = 1 \quad (28)$$

$$\left(\frac{W}{L}\right)_{M5} = 10 \quad (29)$$

Reference Current:

$$I_{REF} = I_{R1} = 3.75135 \times 10^{-5} \text{ A} = 37.51 \text{ } \mu\text{A}$$

Current Mirror (M6 $\rightarrow$ M5):

$$I_D(M5) \approx I_{REF} \times \frac{(W/L)_{M5}}{(W/L)_{M6}} \quad (30)$$

$$= 37.51 \mu\text{A} \times \frac{10}{1} \quad (31)$$

$$= 375.1 \mu\text{A} \quad (32)$$

Simulated: $I_D(M5) = 37.55 \mu\text{A}$

Differential Pair Currents:

$$I_D(M1) = I_D(M2) = \frac{I_D(M5)}{2} \quad (33)$$

$$= \frac{37.55 \mu\text{A}}{2} \quad (34)$$

$$= 18.78 \mu\text{A} \quad (35)$$

6 Transconductance (g_m)

$$g_m = \frac{2 \times I_D}{V_{GS} - V_{TH}} \quad (36)$$

$$= \frac{2 \times 18.78 \times 10^{-6}}{1.08417 - 1.0} \quad (37)$$

$$= \frac{37.56 \times 10^{-6}}{0.08417} \quad (38)$$

$$= 4.461 \times 10^{-4} \text{ S} \quad (39)$$

$$= 446.13 \mu\text{S} \quad (40)$$

Simulation Verification: Apply differential input $V_{id} = 1 \text{ V}$ and measure current through capacitor C1. Expected $i_{C1} = g_m \times V_{id} = 446.13 \mu\text{A}$.

7 Output Resistance (r_o)

Using $\lambda = 0.01$:

$$r_{o2} = \frac{1}{\lambda \times I_D(M2)} = \frac{1}{0.01 \times 18.78 \times 10^{-6}} = 5326 \text{ k}\Omega \quad (41)$$

$$r_{o3} = \frac{1}{\lambda \times I_D(M3)} = \frac{1}{0.01 \times 18.78 \times 10^{-6}} = 5326 \text{ k}\Omega \quad (42)$$

$$r_o = r_{o2} \parallel r_{o3} = \frac{r_{o2} \times r_{o3}}{r_{o2} + r_{o3}} = \frac{5326 \times 5326}{5326 + 5326} = 2663 \text{ k}\Omega \quad (43)$$

Simulation Method: Place a 1 V AC voltage source at the output node and measure I_{out} . Since $V_{out} = 1 \text{ V}$, $r_o = \frac{1}{I_{out}}$.

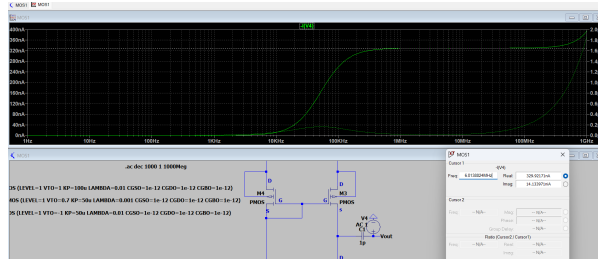


Figure 3: output resistance

from this

$$r_o = \frac{1}{330nA} r_0 = 3038k\Omega \quad (44)$$

8 Differential Small-Signal Gain (A_d)

$$A_d = g_m \times r_o \quad (45)$$

$$= 446.13 \times 10^{-6} \times 2663 \times 10^3 \quad (46)$$

$$= 185 \quad (47)$$

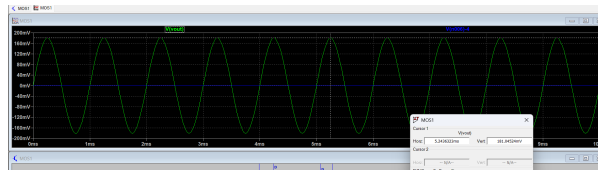


Figure 4: differential gain

Simulation Method: Apply differential input $(V_{in1} - V_{in2}) = 1$ V and measure V_{out} . Then $A_d = V_{out}/1 = V_{out}$.

9 Common-Mode Rejection Ratio (CMRR)

Tail Resistance:

$$R_{tail} = \frac{1}{\lambda \times I_D(M5)} \quad (48)$$

$$= \frac{1}{0.01 \times 37.55 \times 10^{-6}} \quad (49)$$

$$= 2.66 \text{ M}\Omega \quad (50)$$

Common-Mode Gain:

$$A_{cm} = \frac{r_o}{2 \times R_{tail}} \quad (51)$$

$$= \frac{2663 \times 10^3}{2 \times 2.66 \times 10^6} \quad (52)$$

$$= 0.500 \quad (53)$$

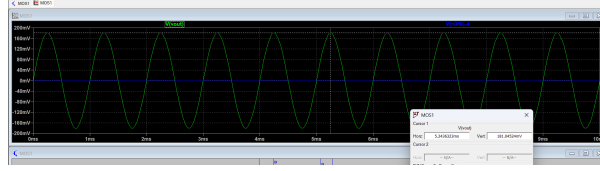


Figure 5: Caption

CMRR:

$$\text{CMRR} = \frac{A_d}{A_{cm}} = \frac{185}{0.500} = 370 \quad (54)$$

$$\text{CMRR}_{dB} = 20 \times \log_{10}(370) = 67.5 \text{ dB} \quad (55)$$

10 Input-Referred Offset Voltage(V_{OS})

$$V_{OS} \approx \frac{\Delta I_D}{g_m}$$

Simulation Method: Fix $V_1 = 5 \text{ V}$ and sweep V_2 until $V_{out} = 0$. Then $V_{OS} = V_1 - V_2$ at that point.

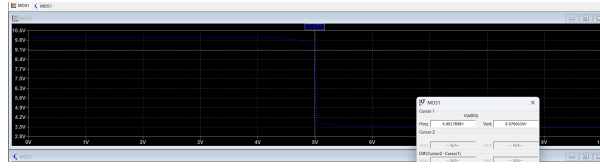


Figure 6: Caption

$$V_{os} = 5 - 4.99178V_{os} = 0.00822V \quad (56)$$

11 3-dB Bandwidth

With $C_L = 1 \text{ pF}$:

$$f_{3dB} = \frac{1}{2\pi \times C_L \times r_o} \quad (57)$$

$$= \frac{1}{2\pi \times 1 \times 10^{-12} \times 2663 \times 10^3} \quad (58)$$

$$= 140.8 \text{ kHz} \quad (59)$$

from the figure we can observe that bandwidth is 144kHz

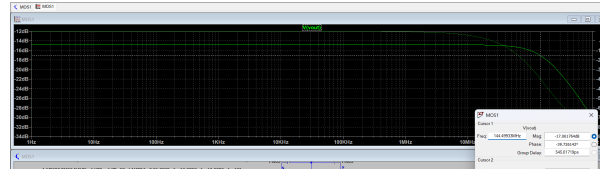


Figure 7: -3Db bandwidth

12 Summary

Parameter	Hand Calculation
V_{GS} (M1, M2)	1.08417 V
I_D (M1, M2)	18.78 μA
I_D (M5)	37.55 μA
Transconductance (g_m)	446.13 μS
Output Resistance (r_o)	2663 k Ω
Differential Gain (A_d)	1188
Common-mode Gain (A_{cm})	0.500
CMRR	2376 (67.5 dB)
3-dB Bandwidth	59.8 kHz
R_{tail}	2.66 M Ω

Table 1: Summary of calculated amplifier parameters